

24/08/23


TEEE

Assignment-1


S. Praveen Kumar

ch.en.v4aie22048 AIE

(1)

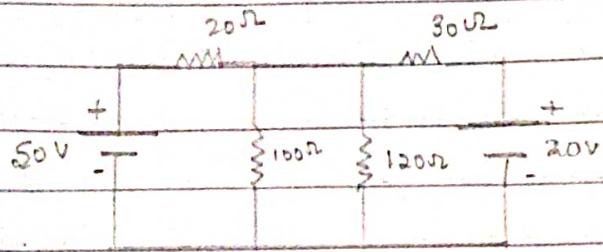

⇒ Solution:-

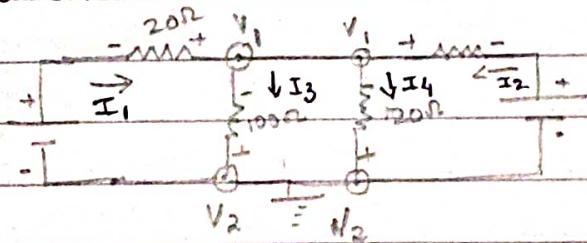here, V_2 is reference nodeApply KCL at node 1 → V_1 .

$$I_1 + I_2 = I_3 + I_4$$

$$\frac{50 - V_1}{20} + \frac{20 - V_1}{30} = \frac{V_1}{120} + \frac{V_1}{100}$$

$$\frac{50 - V_1}{2} + \frac{20 - V_1}{2} = \frac{V_1}{120} + \frac{V_1}{10}$$

$$\frac{150 - 3V_1 + 40 - 2V_1}{6} = \frac{10V_1 + 12V_1}{120}$$

$$20(190 - 5V_1) \cancel{20} = 22V_1$$

$$3800 - 100V_1 = 22V_1$$

$$122V_1 = 3800$$

$$V_1 = 31.143V$$


the voltage through 12Ω

$$I_4 = \frac{V_1}{12\Omega}$$


$$= \frac{31 - 147}{120}$$

$$I_4 = 0.25A$$

(2)

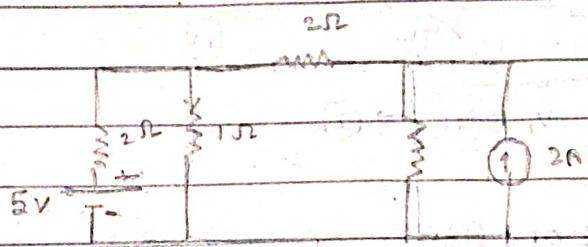

\Rightarrow Solution :-

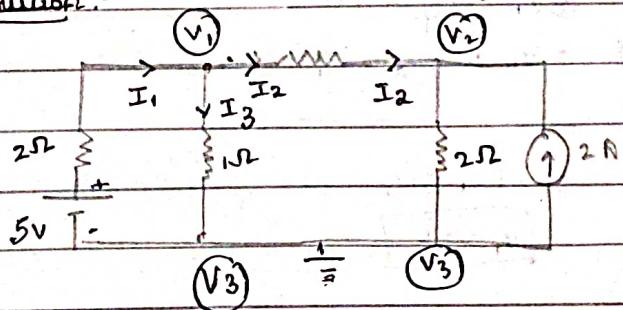

here, v_3 is reference node

$$V_3 = 0$$

Apply KCL at V_1 :-

$$I_1 = I_2 + I_3$$

$$\frac{5 - V_1}{2} = \frac{V_1 - V_2}{2} + \frac{V_1 - 0}{1}$$

$$\frac{5 - V_1}{2} = \frac{V_1 - V_2}{2} + 2V_1$$

$$4V_1 - V_2 = 5 \rightarrow ①$$

Apply KCL at v_2

$$I_2 + I_4 = I_5$$

$$\frac{v_1 - v_2}{2} + 2 = \frac{v_2 - 0}{2}$$

$$\frac{v_1 - v_2 + 4}{2} = \frac{v_2}{2}$$

$$2v_2 - v_1 = 4 \rightarrow (2)$$

from eq (1) and (2)

$$(1) \times 2 \Rightarrow 8v_1 - 2v_2 = 10$$

$$(2) \Rightarrow -v_1 + 2v_2 = 4$$

$$7v_1 = 14$$

$$v_1 = 2V$$


$$v_2 = 3V$$

I_3 is the current through 1Ω resistor


$$I_3 = \frac{v_1 - 0}{1}$$

$$I_3 = 2A$$

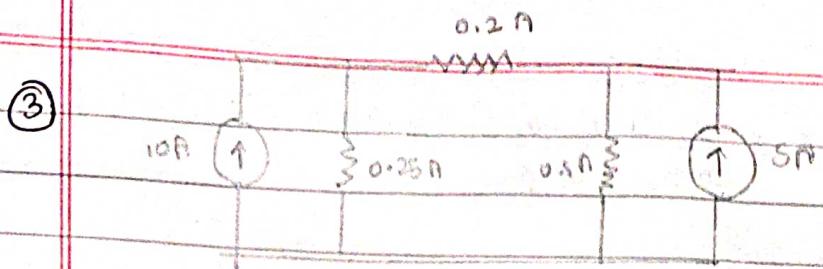\therefore Value of current through 1Ω resistor is '2A'



Solution:-

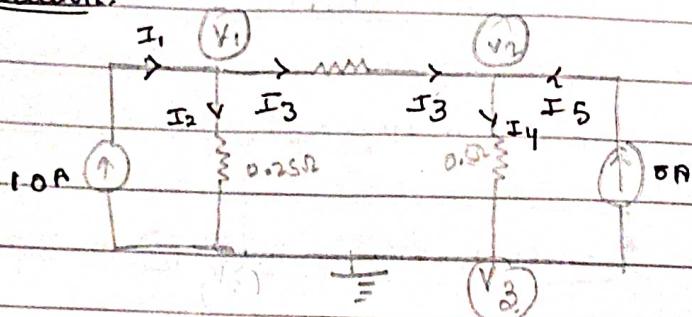

Here, taking v_3 as reference node

$$v_3 = 0V$$

Apply KCL at node v_1

$$I_1 = I_2 + I_3$$

$$I_1 = 10A, \quad I_2 = \frac{v_1 - 0}{0.25}, \quad I_3 = \frac{v_1 - v_2}{0.2}$$

$$10 = \frac{v_1 - 0}{0.25} + \frac{v_1 - v_2}{0.2}$$

$$10 = (0.2)(v_1) + (0.25)v_1 - (0.25)v_2 \\ 0.05$$

$$0.5 = (0.45)v_1 - (0.25)v_2 \rightarrow ①$$

Apply KCL at node v_2

$$I_5 = 5A$$

$$I_3 + I_4 = I_5$$

$$\frac{v_1 - v_3}{0.2} + 5 = \frac{v_2 - 0}{0.5}$$

$$5 = \frac{v_2 + v_2 - v_1}{0.5 - 0.2}$$

$$5 = \frac{(0.2)v_2 + (0.5)v_2 - (0.5)v_1}{0.1}$$

$$0.5 = 0.7v_2 - 0.5v_1$$

$$\boxed{-0.5v_1 + 0.7v_2 = 0.5} \rightarrow \textcircled{2}$$

from eqn $\textcircled{1}$ and $\textcircled{2}$

$$v_1 = \frac{0.7v_2 - 0.5}{0.5}$$

$$\boxed{v_1 = 2.5V}$$

$$\boxed{v_2 = 2.5V}$$

current through:

$$0.2\Omega \Rightarrow I_3 = \frac{v_1 - v_2}{0.2}$$
$$= 0A$$

$$0.25\Omega \Rightarrow I_2 = \frac{v_1}{0.25}$$

$$= \frac{2.5}{0.25}$$


$$\Rightarrow 10A$$

$$0.5\Omega \Rightarrow I_4 = \frac{V_1}{0.5}$$


$$= \frac{2.5}{0.5}$$

$$= 5A$$

4)

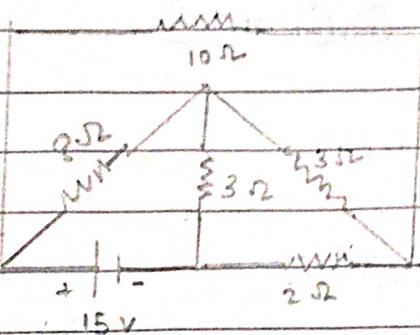

Solution :-

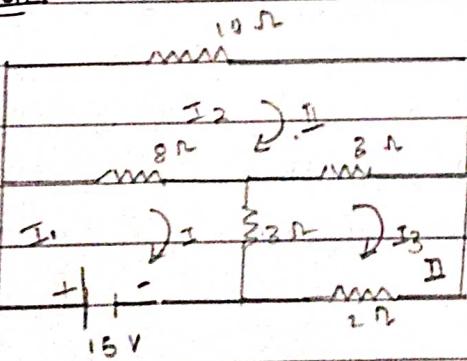

Apply KVL at mesh ①

$$-15 + (I_1 - I_2) 8 + (I_1 - I_3) 3 = 0$$

$$\boxed{11I_1 - 8I_2 - 3I_3 = 15} \rightarrow ①$$

Apply KVL at mesh ②

$$10I_2 + (I_2 - I_3) 3 + (I_2 - I_1) 8 = 0$$

$$21I_2 - 3I_3 - 8I_1 = 0$$

$$\boxed{-8I_1 + 21I_2 - 3I_3 = 0} \rightarrow ②$$

Apply KVL at mesh ③

$$(I_3)2 + (I_3 - I_1)3 + (I_3 - I_2)3 = 0$$

$$I_3 - 3I_1 - 3I_2 = 0$$

$$3I_1 + 8I_2 - 8I_3 = 0 \rightarrow ③$$

from eqn. ①, ② and ③

$$I_1 = 2.63A$$

$$I_2 = 1.21A$$


$$I_3 = 1.44A$$

current through


10Ω is $0.1.21A$.

2Ω is $1.44A$.

(5)

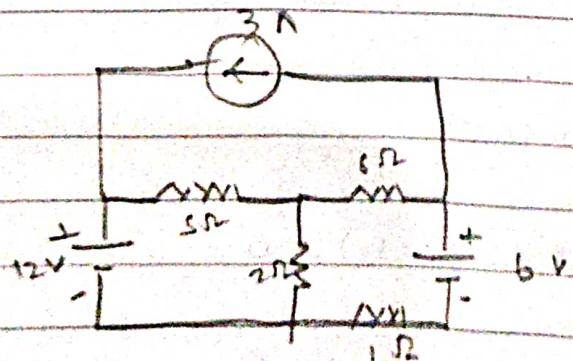

Solution:-

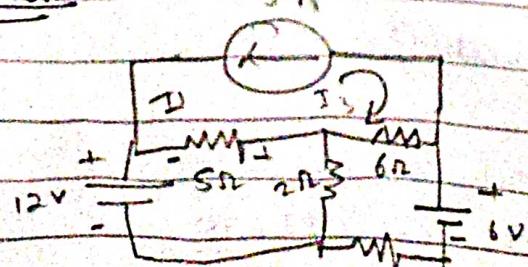

mesh(1)

$$-12 + 5(I_1 - I_2) + 2(I_1 - I_3) = 0$$

$$-12 + 5I_1 - 5I_2 + 2I_1 - 2I_3 = 0$$

$$-12 + 7I_1 - 5I_2 - 2I_3 = 0$$

$$7I_1 - 5I_2 - 2I_3 = 12 \rightarrow (1)$$

mesh(2) :-

$$I_2 = -3A$$

$$7I_1 - 5I_2 - 2I_3 = 12$$

$$7I_1 - 2I_3 = 12 - 15$$

$$\boxed{7I_1 - 2I_3 = -3} \rightarrow (2)$$

mesh(3)

$$6(I_3 - I_2) + 6 + I_3 + 2(I_3 - I_1) = 0$$

$$-2I_1 - 6I_2 + 9I_3 = -6$$

$$\boxed{2I_1 - 6I_2 - 9I_3 = -6} \rightarrow (3)$$

equation(3)

$$2I_1 - 6I_1 - 6I_2 - 9I_3 = -6$$

$$2I_1 - 9I_3 = -6 - 18$$

$$2I_1 - 9I_3 = -6 - 18$$

$$\boxed{2I_1 - 9I_3 = -24} \rightarrow (4)$$

Showing (1) and (4)

$$I_1 = 0.355A$$

$$I_2 = -3A$$

$$I_3 = 2.745A$$



current through

$$IS\Omega \approx 3.3A \quad I_{12} \approx 2.745A$$

$$I_{6\Omega} = 5.44A$$

$$I_{12} \approx 2.745A$$

(6)

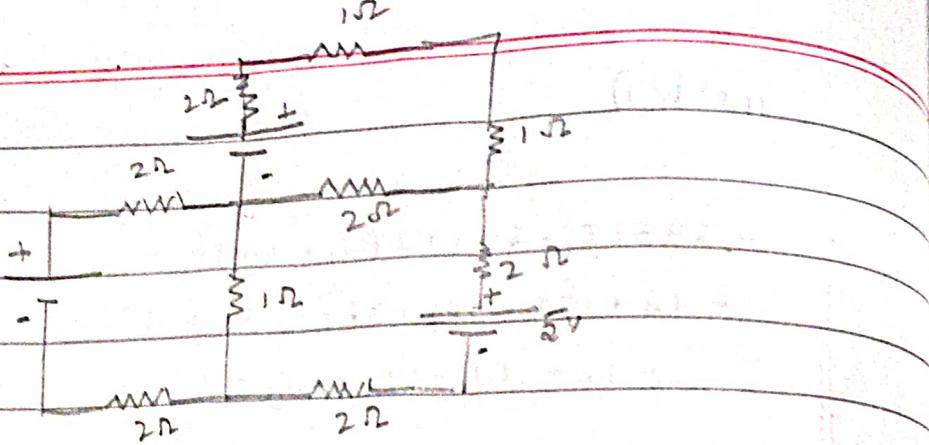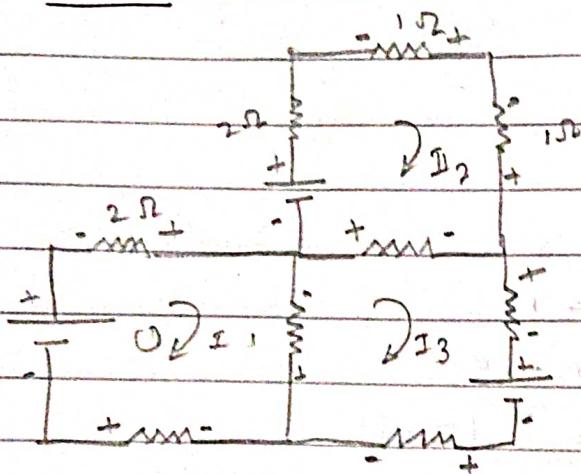Solution :-

Apply KVL at mesh (1) :-

$$2(I_1) + 2(I_1) + (I_1 - I_3) = 5$$

$$5I_1 - I_3 = 5 \rightarrow (1)$$

Apply KVL at mesh (2) :-

$$2I_3 + I_2 + I_2 + (I_2 - I_3) = 5$$

$$6I_2 - 2I_3 = 5 \rightarrow (2)$$

Apply KVL at mesh (3) :-

$$2(I_3 - I_2) + 2I_3 + 5 + 2I_3 + (I_3 - I_1) = 0$$

$$7I_3 - 2I_2 - I_1 = -5 \rightarrow (3)$$

from the eqn (1) and (2), (3)

$$I_1 = 0.913 \text{ A}$$

$$I_2 = 0.706 \text{ A}$$

$$I_3 = -0.380 \text{ A}$$

Current through

mesh (1) \rightarrow

$$I_{2n} = 0.913 \text{ A}$$

$$I_{1n} = 1.29 \text{ A}$$

$$I_{3n} = 0.913 \text{ A}$$

mesh (2)

$$I_{2n} = 0.706 \text{ A}$$


$$I_{1n} = 0.706 \text{ A}$$

mesh (3)

$$I_{2n} = 0.380 \text{ A}$$

$$I_{1n} = 0.380 \text{ A}$$


(3)

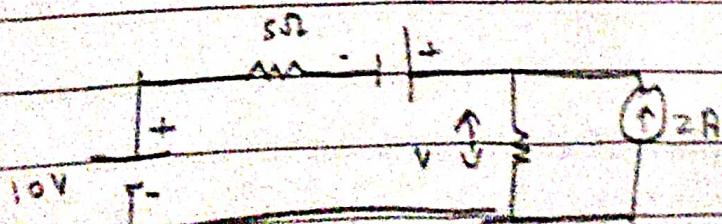

Solution :-

Using Superposition theorem,

case 1 :-

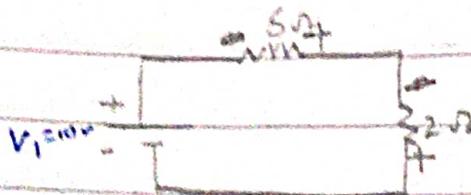

$$V_1 = I_1 R_1$$


$$R = 2 + 5$$

$$= 7 \Omega$$

$$I_1 = \frac{V_1}{R} = \frac{10}{7} = 1.42 A$$

$$\boxed{I_1 = 1.42 A}$$

case 2 :-

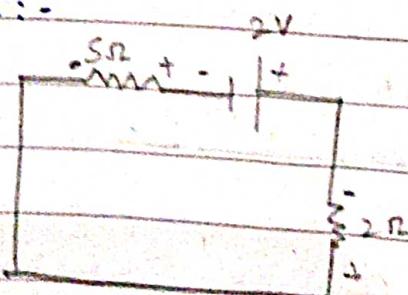


$$V_2 = I_2 R_2$$

$$R = 2 + 5 = 7 \Omega$$

$$I_2 = \frac{V_2}{R} = \frac{2}{7}$$

$$\boxed{I_2 = 0.28 A}$$

Case 3:

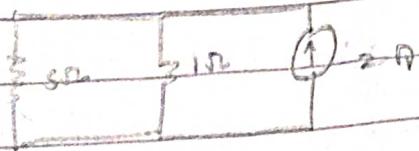

$$\frac{1}{R} = \frac{1}{5} + \frac{1}{2}$$

$$\Rightarrow R_{eq} = \frac{10}{7}$$

$$R_{eq} = 1.42\ \Omega$$

$$V = IR$$

$$V = 2.84\ V$$


Superposition theorem:-

$$V = V_{1,ov} + V_{2,ov} - V_2 A$$

$$= 0.285 + 0.56 - 2.85$$


$$V = 2.01\ V$$

8)

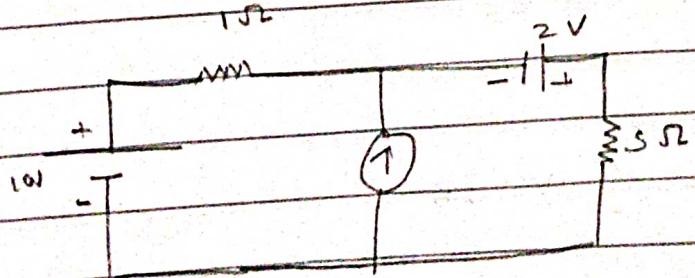

Solution:-

Case 1:

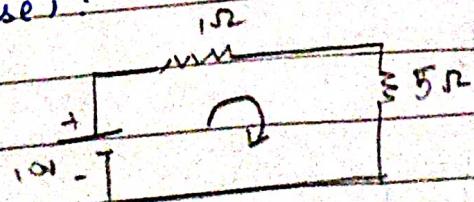

at 1 Ω

$$V = IR$$

$$R = 1 + 5 = 6\ \Omega$$


$$I = \frac{15}{6} = \frac{5}{3}\ A$$

Voltage is

$$[\frac{5}{3} V] \downarrow$$

$$I = \frac{10}{6} = \frac{5}{3}\ A$$

case 2:

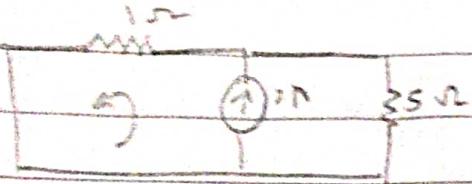

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{25}$$


$$R_{eq} = \frac{5}{6} \Omega$$

$$V = IR \\ = (2) \left(\frac{5}{6} \right)$$

$$V = \frac{5}{3} V$$

\therefore voltage 1Ω is $\left[\frac{5}{3} V \right] \downarrow$

case 3:

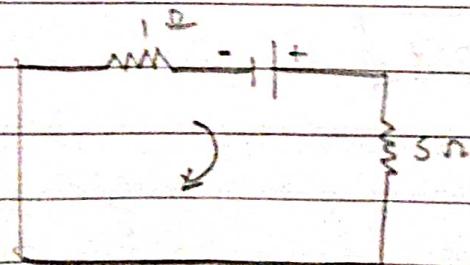

$$V = IR$$

$$3 = I(6)$$

$$I = \frac{1}{3} A$$

at 1Ω

$$\frac{1}{3} = V(1)$$

$$V = \frac{1}{3} V$$

voltage at 1Ω $\left[\frac{1}{3} V \right] \downarrow$

the total voltage at 1Ω resistor is $\Rightarrow \left[\frac{1}{3} + \frac{5}{3} - \frac{5}{3} \right] V$

$$\Rightarrow \frac{1}{3} V$$

$$V_{1\Omega} \Rightarrow 0.33V$$